

**SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA**  
**Minor-I (Even Semester) – 2018-19**

Entry No:

17BEC033

Total number of pages: 01

Total number of questions: 04

B.Tech. || ECE || Sem IV

**Linear Integrated Circuits & Applications (ECL-2030)**

Time allowed: 1.5 Hr

Max Marks: 20

**Important Instructions:**

- All questions are compulsory
- Sketch the schematics whenever necessary
- Assume any missing data

- Q. 1. (a) Derive the expression for CMRR in a dual input balanced output differential amplifier. [3+1+ CO1  
1]
- (b) Note down four ideal characteristics of op-amp. CO2
- (c) Draw and explain the voltage transfer characteristics of op-amp. CO2
- Q. 2. (a) What is the difference between constant current bias and constant current source? [1+3+ CO1  
2]
- (b) Derive the expression of emitter resistance in Widlar current mirror. If  $I_{C1}=1.5$  mA and  $I_{C2}=0.01$  mA, then find out the value of emitter resistance. CO1
- (c) Define the following terms: (a) Input bias current (b) Supply voltage rejection ratio CO2
- Q. 3. (a) Why frequency compensation is necessary in op-amp for stable operation? [1+2+ CO2  
1]
- (b) A non-compensated op-amp has a dc gain of 120000 and the break frequencies at 30 KHz and 200 KHz. Write down the open loop gain equation for op-amp as a function of break frequencies. Also find out the operating frequency at which gain will be 30 dB. CO2
- (c) For a noninverting feedback op-amp with a single break frequency has unity gain bandwidth product of 10 MHz and closed loop gain of 100. What is the value of closed loop gain at the break frequency?
- Q. 4. (a) Why negative feedback is necessary in an op-amp circuit? Derive the modified expression for basic parameters, affected by voltage series feedback op-amp circuit. [3+2] CO1
- (b) If  $R_i=2$  M $\Omega$ ,  $R_O=60$   $\Omega$ ,  $R_1=2$  K and  $R_F=30$  K for IC 741 op-amp, then calculate the feedback parameters in a non-inverting op-amp. [consider all standard notations] CO1

Sl. No.	Course outcome	Q. No.	Total marks
1.	To understand the design concepts of Operational amplifier IC	1 (a), 2 (a, b), 4	12
2.	To understand the basic characteristics of op-amp	1 (b, c), 2 (c), 3	8