

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA
School of Electronics & Communication Engineering
B. Tech. 4th Minor-I Examination (Even) 2018-19

Entry No: 1 7 13 E C 0 3 3

Date:

Total Number of Pages: [01]

Total Number of Questions: [06]

Course Title: Digital System Design using VERILOG
Course Code: ECL 2073

Time Allowed: 1.5 Hours

Max Marks: [20]

Instructions / NOTE

- i. Attempt All Questions.
- ii. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- iii. Assume an appropriate data / information, wherever necessary / missing.
- iv. Use of IS Code (Mention Number) is permissible in examination.

Section - A			
Q1.	(a) Verilog HDL is a programming Language (TRUE/ FALSE) (b) Verilog HDL is case-insensitive (TRUE/ FALSE) (c) Default data-type of port names is _____ (d) Object names must be started with _____ (e) An object of REG data-type can assigned a value in _____ (f) Name the two Verilog primitives which has more than one output.	[03]	CO1
Q2.	(a) Name the value sets used in Verilog HDL, and describe in one line how they are used in Verilog. (b) What values are assigned to left hand side object on its execution if B = 'b 0101_1101_1011 and C = 'h ABCD ? (c) A = ~& (B) ; (ii) A = & (~B) ; (iii) A = B & (~C) ;	[02] [03]	CO2 CO2
Q3.	Describe the capabilities of Verilog-HDL (write point-wise)	[03]	CO1
Section - B			
Q4.	Design a Verilog-HDL module for 3:8 Decoder using data-flow modeling.	[03]	CO2
Q5.	Write a Verilog Test-Bench code to apply inputs to a 2-bit full adder circuit. (module name is fa_2bit with ports in this sequence (sum, cout, a in, b in, c in))	[02]	CO4
Q6.	Design a Verilog module for 2:1 mux using gate-level modeling. Then use that 2:1 mux to design a module for 8:1 mux. (Must be supported with Block/circuit diagrams)	[04]	CO3

Course Outcomes

- CO 1: Describe Verilog hardware description languages (HDL).
 CO 2: Design Digital Circuits and Write behavioral models of digital circuits.
 CO 3: Write Register Transfer Level (RTL) models of digital circuits.
 CO 4: Verify behavioral and RTL models.

CO	Questions Mapping	Total Marks	Total Number of Students (to be appeared in Exam)
CO1	Q1, Q3	06	61
CO2	Q2, Q4	08	61
CO3	Q6	04	61
CO4	Q5	02	61

NO of copies = 70 security only

Entry No:

17BEC033

Total Number of Pages: [01]

Date:

Total Number of Questions: [05]

Course Title: Digital System Design using VERILOG

Course Code: ECL-2073

Time Allowed: 1.5 Hours


Max Marks: [20]

Instructions / NOTE

- Attempt All Questions.
- Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- Assume an appropriate data / information, wherever necessary / missing.

Section - A

Q1.	Explain different loop-statements with using short examples	[04]	CO1
Q2.	Write Verilog code for Figure shown below using case-statement and if-statement.	[05]	CO2

 

Section - B

Q3.	Design a Verilog module for 8:3 priority encoder using case statement.	[03]	CO2
Q4.	Design a Verilog module design 5-bit synchronous (+ve edge Triggered) multiplier with asynchronous active HIGH RESET. When reset, the output should be equal to zero. (Draw External-view also)	[04]	CO3
Q5.	Design a Verilog module for negative edge triggered modulo-12 down- counter with asynchronous active low RESET and synchronous LOAD facility. (When Load = LOW, then output is will be loaded with Data_in, else works as normal down-counter). (Draw External-view also)	[04]	CO3

Course Outcomes

- CO 1: Describe Verilog hardware description languages (HDL).
CO 2: Design Digital Circuits and Write behavioral models of digital circuits.
CO 3: Write Register Transfer Level (RTL) models of digital circuits.
CO 4: Verify behavioral and RTL models.

CO	Questions Mapping	Total Marks	Total Number of Students (to be appeared in Exam)
CO1	Q1	04	61
CO2	Q2, Q3	08	61
CO3	Q4, Q5	08	61
CO4			

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA

School of Electronics & Communication Engineering

B. Tech. 4th Major Examination (Even) 2018-19 May-2019

Entry No:

17BEC033

Total Number of Pages: [02]

Date:

Total Number of Questions: [10]

Course Title: Digital System Design using VERILOG

Course Code: ECL-2073

Time Allowed: 1.5 Hours


Max Marks: [20] D

Instructions / NOTE


- Attempt All Questions.
- Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- Assume an appropriate data / information, wherever necessary / missing.

Section - A

Q1	A digital circuit $f(A,B,C)$ gives a LOW output signal for a given input combination. However, when there occurs a change in the input signals (i.e., A,B,C), the output signal switches from LOW to HIGH and then came back to LOW. What type of hazard the circuit does have? Comment and give remedy for this type of circuit by taking an example.	2.5	CO1																																																																						
Q2	<p>A digital designer has to design the following ROM like circuit for the table given below.</p> <table><thead><tr><th colspan="3">Inputs</th><th colspan="4">Outputs</th></tr><tr><th>A_2</th><th>A_1</th><th>A_0</th><th>D_3</th><th>D_2</th><th>D_1</th><th>D_0</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr></tbody></table> <p>Write Verilog module for this circuit, so that ROM will infer from Verilog synthesis process.</p>	Inputs			Outputs				A_2	A_1	A_0	D_3	D_2	D_1	D_0	0	0	0	1	1	1	1	0	0	1	1	1	1	0	0	1	0	1	1	0	1	0	1	1	1	1	0	0	1	0	0	1	0	1	1	1	0	1	1	0	1	0	1	1	0	1	0	0	1	1	1	1	1	0	0	0	2.5	CO2
Inputs			Outputs																																																																						
A_2	A_1	A_0	D_3	D_2	D_1	D_0																																																																			
0	0	0	1	1	1	1																																																																			
0	0	1	1	1	1	0																																																																			
0	1	0	1	1	0	1																																																																			
0	1	1	1	1	0	0																																																																			
1	0	0	1	0	1	1																																																																			
1	0	1	1	0	1	0																																																																			
1	1	0	1	0	0	1																																																																			
1	1	1	1	0	0	0																																																																			
Q3	<p>(a) What is the difference between a Moore and Mealy Machine?</p> <p>(b) What are similarities and differences between forever-loop and repeat-loop?</p>	02	CO1																																																																						
Q4	Write five main differences between a function and a task .	04	CO1																																																																						
Q5	Design $\sum(A, B, C) = (0, 1, 5, 7)$ using PAL circuit.	03	CO3																																																																						
Q6	Draw the block diagram of an FPGA chip and explain the functionality of each block.	04	CO1																																																																						
Section – B																																																																									
Q7	Write Verilog code for Figure shown below using case-statement and if-statement and also write a test-bench for the same.	07	CO4																																																																						

 


 - Q8 Write a Verilog module that receives a clock signal (CLK), and reset signal (RST) and generates two clock signals CLK_div_8 (1/8 th of CLK) and CLK_div_32 (1/32 th of CLK)



- Q9 A sequence detector is to detect "110001" non-overlapped sequence and gives a LOW output signal when detected successfully. Design a state-machine and state-table for this sequence detector and write its verilog-code.

 - Q10 Write a verilog module using FUNCTIONS for the circuit given below.



The circuit gives 1's complement of Data_in at Data_out lines and OE = LOW when Data_in contains even number of ones. Similarly it gives 2's complement of Data_in at Data_out lines and OE = HIGH when Data_in contains odd number of ones. Note that the whole process is carried out at +ve edge of the CLK.

Course Outcomes

- CO 1: Describe Verilog hardware description languages (HDL).
 CO 2: Design Digital Circuits and Write behavioral models of digital circuits.
 CO 3: Write Register Transfer Level (RTL) models of digital circuits.
 CO 4: Verify behavioral and RTL models.

CO	Questions Mapping	Total Marks	Total Number of Students (to be appeared in Exam)
CO1	Q1,Q3,Q4,Q6	14.5	61
CO2	Q2,Q9	10.5	61
CO3	Q5,Q8,Q10	18	61
CO4	Q7	07	61