

**SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA**  
**School of Electrical & Civil Engineering**  
**B. Tech. Minor-II, 2019-20**

Entry No: 1 8 8 E E 0 2 1

Date: 30-09-2019

Total Number of Pages: [01]

Total Number of Questions: [06]

Course Title: Electrical Machine-I

Course Code: EEL 2321

Time Allowed: 1.5 Hours

Max Marks: [30]

Instructions / NOTE

- i. Attempt All Questions. Scientific Calculator is allowed in this paper.
- ii. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- iii. Assume an appropriate data / information, wherever necessary / missing.

Q1 ✓	Derive the equation for induced EMF on primary side and secondary side in a two winding single phase transformer.	[05]
Q2 ✓	Draw and explain the phasor diagram of a transformer with winding resistance but no magnetic leakage with unity power factor load on secondary side.	[05]
Q.3.	The equivalent circuit for a 200/400-V step-up transformer has the following parameters referred to the low-voltage side. Equivalent resistance = $0.15 \Omega$ ; Equivalent reactance $0.37 \Omega$ Core-loss component resistance $600 \Omega$ ; Magnetising reactance $300 \Omega$ When the transformer is supplying a load at 10 A at a power factor of 0.8 lag, calculate the primary current.	[05]
Q.4.	Determine the core area, the number of turns and the position of the tapping point for a 500-kVA, 50-Hz, single-phase, 6.600/5.000-V auto-transformer, assuming the following approximate values : e.m.f. per turn 8 V, Maximum flux density $1.3 \text{ Wb/m}^2$ .	[05]
Q.5 ✓	Explain fully with help of diagram <i>scott</i> connection in transformer and why we need this connection?	[05]

Q.6.	A 100-kVA, 3-phase, 50-Hz 3,300/400 V (Line voltage) transformer is $\Delta$ -connected on the h.v. side and Y-connected on the l.v. side. The resistance of the h.v. winding is $3.5 \Omega$ per phase and that of the l.v. winding $0.02 \Omega$ per phase. Calculate the iron losses of the transformer at normal voltage and frequency if its full-load efficiency be 95.8% at 0.8 p.f. (lag).	[05]
------	--	------