

# SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA

Minor-I (Even Semester) - 2018-19

Entry No:

17BEC033

Total number of pages: 01

Total number of questions: 04

B.Tech. || ECE || Sem IV

## Linear Integrated Circuits & Applications (ECL-2030)

Time allowed: 1.5 Hr

Max Marks: 20

### Important Instructions:

- All questions are compulsory
- Sketch the schematics whenever necessary
- Assume any missing data

- Q. 1. (a) Derive the expression for CMRR in a dual input balanced output differential amplifier. [3+1+ CO1  
1]
- (b) Note down four ideal characteristics of op-amp. CO2
- (c) Draw and explain the voltage transfer characteristics of op-amp. CO2
- Q. 2. (a) What is the difference between constant current bias and constant current source? [1+3+ CO1  
2]
- (b) Derive the expression of emitter resistance in Widlar current mirror. If  $I_{C1}=1.5$  mA and  $I_{C2}=0.01$  mA, then find out the value of emitter resistance. CO1
- (c) Define the following terms: (a) Input bias current (b) Supply voltage rejection ratio CO2
- Q. 3. (a) Why frequency compensation is necessary in op-amp for stable operation? [1+2+ CO2  
1]
- (b) A non-compensated op-amp has a dc gain of 120000 and the break frequencies at 30 KHz and 200 KHz. Write down the open loop gain equation for op-amp as a function of break frequencies. Also find out the operating frequency at which gain will be 30 dB. CO2
- (c) For a noninverting feedback op-amp with a single break frequency has unity gain bandwidth product of 10 MHz and closed loop gain of 100. What is the value of closed loop gain at the break frequency?
- Q. 4. (a) Why negative feedback is necessary in an op-amp circuit? Derive the modified expression for basic parameters, affected by voltage series feedback op-amp circuit. [3+2] CO1
- (b) If  $R_i=2$  M $\Omega$ ,  $R_O=60$   $\Omega$ ,  $R_1=2$  K and  $R_F=30$  K for IC 741 op-amp, then calculate the feedback parameters in a non-inverting op-amp. [consider all standard notations] CO1

Sl. No.	Course outcome	Q. No.	Total marks
1.	To understand the design concepts of Operational amplifier IC	1 (a), 2 (a, b), 4	12
2.	To understand the basic characteristics of op-amp	1 (b, c), 2 (c), 3	8



# SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA

Minor-II (Even Semester) – 2018-19

Entry No:

--	--	--	--	--	--	--	--

Total number of pages: [01]

Total number of questions: 04

B.Tech. || ECE || Sem IV

## Linear Integrated Circuits & Applications (ECL-2030)

Time allowed: 1.5 Hr

Max Marks: 20

### Important Instructions:

- All questions are compulsory
- Sketch the schematics whenever necessary
- Assume any missing data

- Q. 1. (a) Draw the circuit diagram and explain the working of a square wave generator. Also Design a square wave generator for 1 KHz frequency. [3+2] COI
- Q. 2. (a) Explain the working of a practical differentiator. Why it is beneficial over ideal differentiator. [3+2] COI
- (b) Design a practical differentiator with cutoff frequency of 8 KHz. COI
- Q. 3. (a) Drive the expression for output voltage of an instrumentation amplifier. [2+3] COI
- (b) Draw the circuit diagram and output waveform for each op-amp applications listed below. Assume 2 V peak and 1 KHz frequency sinusoidal signal as input for all applications. COI
- (a) Positive clipper (b) Sample & hold Circuit (c) Schmitt Trigger
- Q. 4. (a) Determine the output voltage for the following 3 circuits shown in figure 1-3. Assume all standard notations. [2+2+1] COI

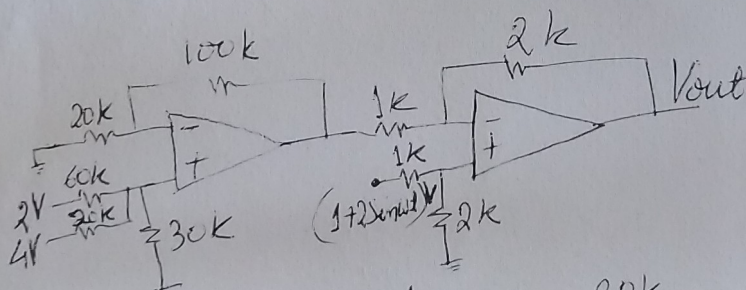


Figure - 1

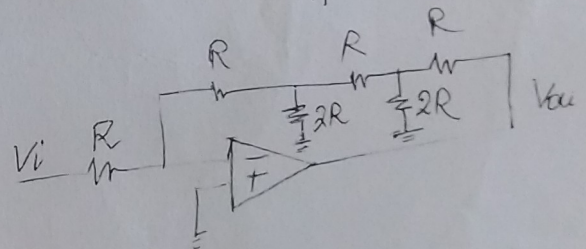


Figure - 2

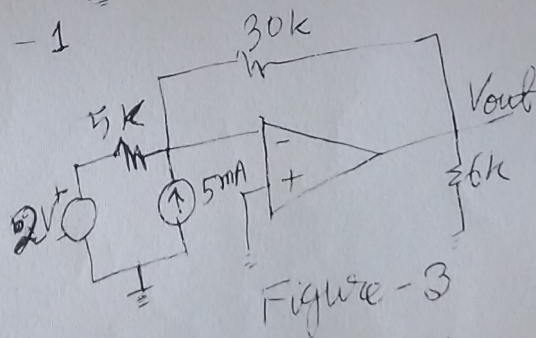


Figure - 3

Sl. No.	Course outcome	Q. No.	Total marks
1.	To be able to design some basic linear and nonlinear circuits using op-amp.	1 -4	20



**SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA**  
Major Examination (Even Semester) – 2018-19

Entry No:

17B E C 0 3 3

Total number of pages: [02]

Total number of questions: [04]

B.Tech. || ECE || Sem IV

## Linear Integrated Circuits & Applications

Subject Code: ECL-2030

Time allowed: 3 Hr

Max Marks: 50

Important Instructions:

- All questions are compulsory
- Assume any missing data
- Sketch schematics whenever needed

- Q1. (i) Why op-amp circuits are specified as linear integrated circuits? [1×10  
=10] [CO1]
- (ii) Power supply rejection ratio of an ideal op-amp should be \_\_\_\_\_. [CO2]
- (iii) The OP-AMP comparator circuit uses \_\_\_\_\_ feedback. [CO2]
- (iv) The Schmitt trigger can be used as a \_\_\_\_\_ wave generator. [CO2]
- (v) If the output of a particular op-amp increases 6 V in 8μs. The slew rate is \_\_\_\_\_. [CO3]
- (vi) An op-amp has unity gain bandwidth product of 1.5 MHz for a signal of frequency 2 KHz. What is the open loop dc voltage gain? [CO3]
- (vii) Specify the conditions necessary for generations of oscillation in electronic device. [CO4]
- (viii) An integrator can be used as a \_\_\_\_\_ filter. [CO4]
- (ix) Why Butterworth filters are commonly used? [CO4]
- (x) Discharging path through \_\_\_\_\_ is followed by a 555 timer in monostable multivibrator mode. [CO5]
- 
- Q2. (a) Design the following circuits using op-amp and explain their working. [include waveform/graph, if needed] [2+4+4  
+5=15]
- (i) Logarithmic Amplifier [CO2]
- (ii) Triangular wave generator [CO2]
- (iii) Wien bridge Oscillator [CO4]
- (iv) Double feedback narrow band pass filter [CO4]
- 
- (b) Show the following applications of op-amp with neat sketch of circuit diagram and corresponding waveform/graph: [1×5  
=5]
- (i) Scale changer (ii) Voltage limiter (iii) Phase shifter [CO2]
- (iv) Narrow band reject filter (v) RC phase shift oscillator [CO4]



- Q3. (a) What is the difference between Active and passive filters? [1+1+3] [CO4]  
 (b) What are the advantages of Active filters? +3+2  
 (c) Design a second order low pass Butterworth filter whose 3 dB cutoff frequency is 15 KHz. =10] [CO4]  
 (d) With a suitable internal circuit diagram, explain the working of astable multivibrator [CO4]  
 (e) Calculate the duty cycle for the astable multivibrator output, if  $C = 0.01 \mu F$ ,  $R_A = 10 K\Omega$  &  $R_B = 40 K\Omega$ ? [CO5]

- Q4. (a) Find the DC analysis parameters  $[V_{CQ} \& I_{CQ}]$  for differential amplifier as shown in Fig. 1. [2+2] [CO1]  
 (b) Two identical transistors with  $V_{BE} = 0.7 V$  is connected as shown in Fig. 2. Determine the output voltage  $V_0$ . +3+3  
 (c) Find the values of currents as indicated in Fig. 3. =10] [CO1]  
 (d) Design a RC phase shift oscillator for 10 KHz frequency of oscillation. [CO2]  
 [CO4]

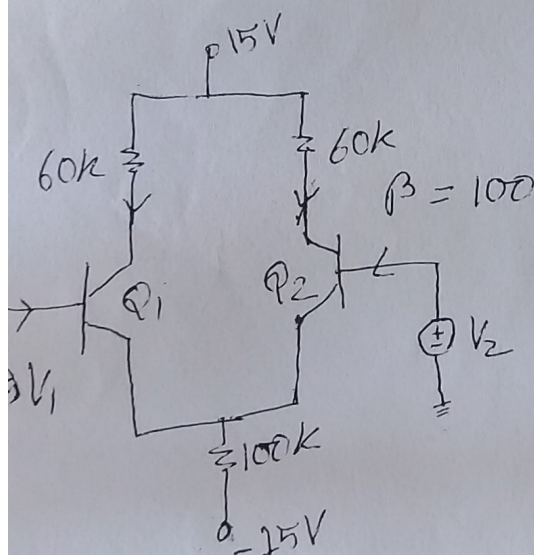


Figure - 1

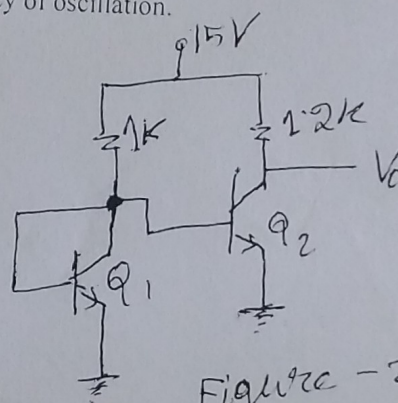


Figure - 2

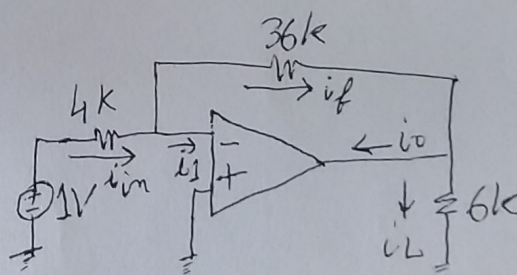


Figure - 3

Sl. No.	Course outcome	Q. No.	Total marks
1.	To understand the concept of differential amplifiers		5
2.	To understand the basics of Operational amplifiers and its applications		14
3.	To be able to perform the Frequency response analysis of Op-amp		2
4.	To be able to design active filters and oscillators using Op-amp		23
5.	To be introduced about some specialized IC applications of OP-amp		6